

Andy Jeong

ECE 150B

Spring 2015

31 March 2015


Project 2: Timing, Multiplexing, and Demultiplexing

Abstract

This project aims to construct a circuit that resembles the functionalities of a 6-channel telegraph system. With 6 inputs through a multiplexer, the output through a demultiplexer is produced at the clock pulses of varying speeds.

Diagram

Image 1 [Top view]

 

Explanation of Design

1. Inventory of parts (#)

- a. Push toggle switch (2 units)
 - i. The function of a push button switch is to toggle a flip flop when closed. Debouncing was not necessary as the toggling of JK flip flop worked fine without it.
- b. 4027 [JK Flip Flop] (4 gates, 2 chips)
 - i. A JK flip flop gate was used to toggle between the two timer speeds with some logic involving an AND and an OR gate. 3 gates were used for counter setup configuration with synchronous clock.
- c. 555 [Astable model] (2 units)
 - i. Calculation of the frequency to meet max. 1 kHz and 0.5 Hz
 - ii. The formula for the frequency of a 555 astable timer is defined as the following:

$$f = 1.44 / [(R1+2R2)C]$$

Therefore,

1. **1 kHz:** $f = 1.44 / [(R1)C]$; $R1 = 1.44 \text{ k}\Omega$, $C = 1.0 \text{ }\mu\text{F}$
2. **0.5 Hz:** $f = 1.44 / [(R1+2R2)C]$; $R1 = 2.7 \text{ M}\Omega$, $R2 = 51 \text{ k}\Omega$, $C = 1.0 \text{ }\mu\text{F}$

The maximum of 1 kHz frequency was met by setting R2, the resistance through a potentiometer, equal to zero. As turning the knob on the potentiometer increases the resistance, this action increases the total resistance value, $R1+2R2$, which then decreases the frequency. Thus, R1 was set to $1.44 \text{ }\Omega$ and $C = 1.0 \text{ }\mu\text{F}$. The frequency is then bounded by the upper limit at 1 kHz. The lower requirement of 0.5 Hz was met by setting $R1 = 2.7 \text{ M}\Omega$, $R2 = 51 \text{ k}\Omega$, and $C = 1.0 \text{ }\mu\text{F}$.

- d. Potentiometer 103 [10k Ω] (1 unit)
 - i. The role of a potentiometer is to be able to adjust the resistance for the timer to change its frequency
- e. 4081 [AND] (4 gates, 1 chip)
 - i. Two as part of the logic to toggle between two timer speeds and to provide an input combination for the counter; one as a logic for counter j, k input; one as a combinational logic for the transducer
- f. 4071 [OR] (2 gates, 1 chip)
 - i. As part of the logic to toggle between two timer speeds and to provide an input combination for the counter; one as a logic for counter j, k input
- g. 4053 [triple 2-bit selector(mux)] (1 chip)
 - i. Used to select between DIP switch inputs and counter inputs, depending upon a designated select switch
- h. 4543 [BCD-decimal decoder] (1 chip)
 - i. Necessary for display on 7-seg display module
- i. 7-segment display (1 unit)
 - i. Necessary for displaying the channel number 1-6
- j. 4051 [Demux]

- i. Needed to produce 6 outputs based on the control bits
- k. 4512 [Mux]
 - i. In order to input 6 data and output 1 single line, to be transferred to the demux
- l. Piezoelectric transducer (1 unit)
 - i. To indicate whether the inputs (HIGH) to the mux have been added by a toggle push button switch
- m. DIP Switch
 - i. To switch between manual and counter modes in counting; to supply LOW for 0 inputs for the selector (mux)
- n. Resistors (330 Ω , 2.1 M Ω , 51 k Ω , 1.5 k Ω)
- o. LED's
- p. Capacitors
 - i. Decoupling, astable timers

Color Coding


- a. Red: Vdd
- b. Gray: clock inputs; inputs to the BCD-to-binary decoder from the 2:1 selector
- c. White: inputs for the j and k's of the jk flip flops for the counter
- d. Blue: OR-ing the timer outputs of different speeds; inputting the decoded outputs into the 7-segment display; inputs for the 2:1 selector (HIGH states)
- e. Orange: inputs for the 2:1 selector (LOW states), DIP switch control inputs into the 2:1 selector, the inputs for both timers until combined in an OR gate; inputs from a toggle push button switch to the multiplexer and transducer activation
- f. Black: Vss

Use of Breadboards

- a. *As highlighted in Image 1, the two breadboards consist of a set of two astable timers, a 3-bit jk flip flop binary counter (1-6), 7 segmented display with a decode, a piezoelectric transducer and a set of mux-demux for transferring data and selecting based on the controls.*
- b. *Two breadboards were used to build a 6-channel telegraph. The positions were determined based on the sequence from the functional block diagram. Although the transducer could have been AND-ed with a new timer to activate a higher pitch, this would require another breadboard allotted just for one purpose. By using a remaining AND gate I was able to put it on the bottom of the first board.*

Design*Counter**State Table*

| Q2 | Q1 | Q0 | Q2 | Q1 | Q0 | J0 | K0 | J1 | K1 | J2 | K2 |
|----|----|----|----|----|----|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 1 | 0 | x | 1 | 1 | X | 0 | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | X | x | 0 | 0 | X |
| 0 | 1 | 1 | 1 | 0 | 0 | x | 1 | x | 1 | 1 | X |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | X | 0 | X | x | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | x | 1 | 1 | X | x | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | X | x | 1 | x | 1 |

 State Diagram

Karnaugh Map

J0 = 1

| | | | | | | | |
|-------|---|----------|--|----|----|----|----|
| | | q_2q_1 | | 00 | 01 | 11 | 10 |
| q_0 | 0 | | | x | 1 | 1 | 1 |
| | 1 | | | x | X | X | X |

K0 = 1

| | | | | | | | |
|-------|---|----------|--|----|----|----|----|
| | | q_2q_1 | | 00 | 01 | 11 | 10 |
| q_0 | 0 | | | x | X | X | X |
| | 1 | | | 1 | 1 | X | 1 |

J1 = Q_0

| | | | | | | | |
|-------|---|----------|--|----|----|----|----|
| | | q_2q_1 | | 00 | 01 | 11 | 10 |
| q_0 | 0 | | | X | x | x | 0 |
| | 1 | | | 1 | x | x | 1 |

K1 = $Q_1 + Q_2$

| | | | | | | | |
|-------|---|----------|--|----|----|----|----|
| | | q_2q_1 | | 00 | 01 | 11 | 10 |
| q_0 | 0 | | | x | 0 | 1 | X |
| | 1 | | | x | 1 | X | X |

$$J2 = Q_0 Q_1$$


| | | 00 | | 01 | | 11 | | 10 | |
|-----|------|----|---|----|---|----|--|----|--|
| q01 | q2q1 | | | | | | | | |
| | 0 | x | 0 | x | x | | | | |
| | 1 | 0 | 1 | x | X | | | | |

$$K2 = Q_1$$


| | | 00 | | 01 | | 11 | | 10 | |
|----|------|----|---|----|---|----|--|----|--|
| q0 | q2q1 | x | x | 1 | 0 | | | | |
| 0 | | x | x | x | 0 | | | | |
| 1 | | | | | | | | | |

Logic Diagram

3-bit Counter using JK Flip Flop

 

Schematic Diagram

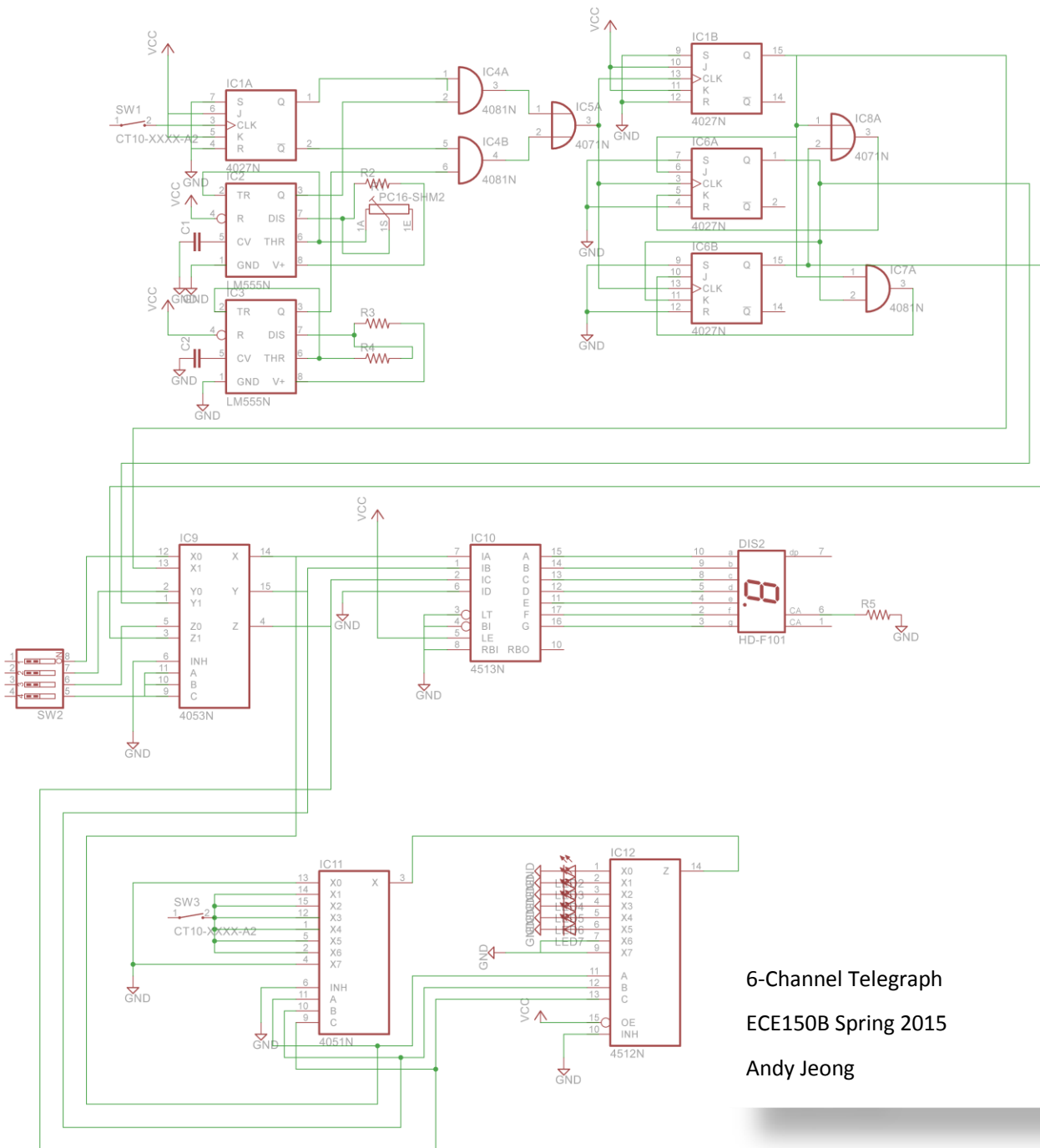

6-Channel Telegraph
ECE150B Spring 2015
Andy Jeong

Functional Block diagram

