

Lab 12 - Voltage Regulator

Junior Projects II - ECE 394A

March 25, 2019

Contents

1	Lab 12.2 - Three Terminal Fixed Regulator	2
2	Lab 12.3 - Adjustable Three-Terminal Regulator: 317	8
3	Lab 12.5 - "Crowbar" Over-Voltage Protection	11
A 78L05 Design		15
B LM317 Design		17
C Thyristor (SCR) Design		19

Partners: Andy Jeong
 Ali Rahman
 Kevin Lin
Instructor: Professor Shlayan

Abstract

In this series of lab experiments, voltage regulated power supply circuits are explored. One of the important characteristics of a voltage regulator, the dropout voltage of a linear type, which is simply the difference between input and output voltage is closely examined - without this characteristic, the output drops out of regulation, and thus the circuit falls out of proper and desired behavior. In addition, management of power dissipation through self-protection in fixed, adjustable regulator circuits is verified through analysis of the IC chip in detail.

Introduction

For the purposes of exploration with voltage regulators throughout this series of experiments, the components 78L05 and 317 have been used. The 317 chip is easier to use and is more versatile than 78L05, with regards to its adjustable output voltage. In addition, it is easier to rig up a current source with ease; for these reasons, this is employed in 12-3: Adjustable Regulator. For simple regulators, 78L05 is easy to implement, protects from current limiting and damage from excessive power dissipation ($I_{out}[V_{in} - V_{out}]$). Prior to currently available fully-integrated regulators, 723 regulators were used, which consist of elements that are standard to a typical regulator: an op amp, "pass" transistors, and a reference voltage, as shown below in Figure 1. Since this is outdated is no longer readily available, experimentation with this chip is omitted.

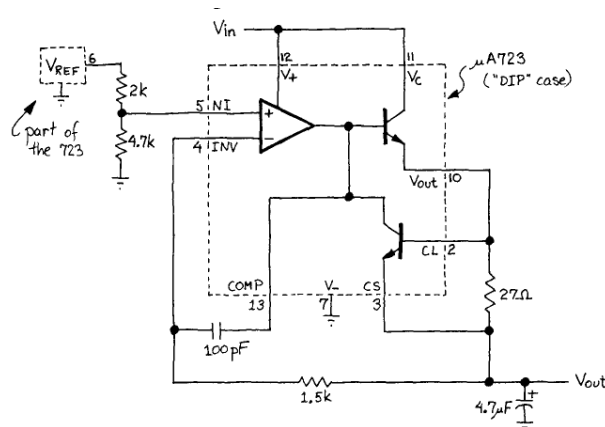


Figure 1: Traditional 723 Voltage Regulator IC Schematic

Experiments

1 Lab 12.2 - Three Terminal Fixed Regulator

 


Figure 2: 78L05 Fixed 3-Terminal Regulator

Three Terminal Fixed Regulator

78L05 is an easy 3-terminal fixed (non-adjustable) regulator, that prevents from current limiting and excessive power dissipation. Upon dealing with this device, one should observe continued heat sinking effect due to power dissipation. In order to observe this heat sinking effect, a resistive load that draws less than the chip's maximum amount of current (100mA) is added on one end - namely 120Ω resistors in parallel, providing 60Ω. As per the datasheet for 78L05 chip, a common ground is required between the input and the output voltages. and the input voltage must remain typically 2.0 V above the output voltage even during the low point on the input ripple voltage. Therefore, as seen in Figure 2, the negative terminal of the variable supply is kept in float, not tied to common ground.

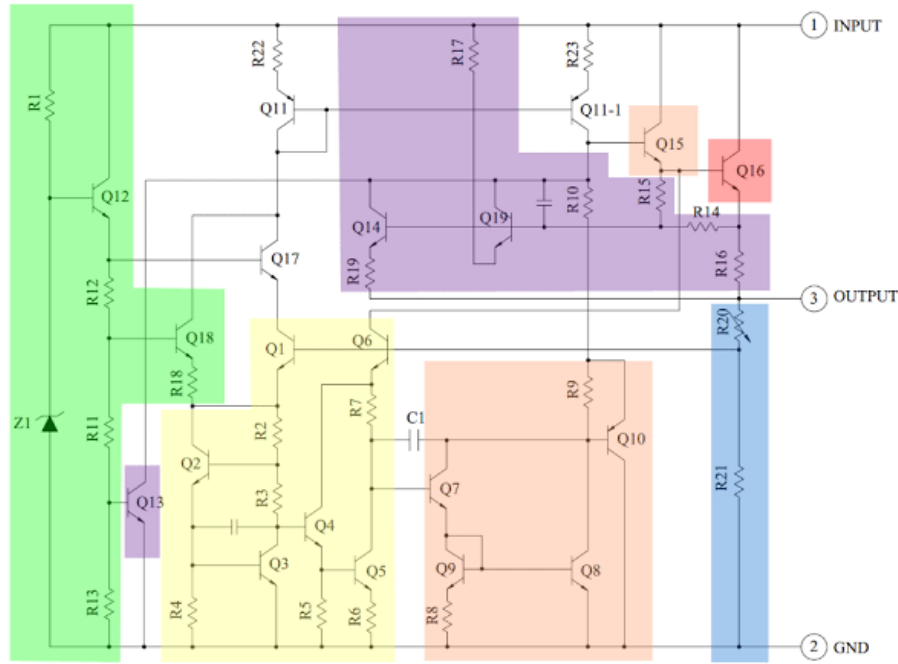


Figure 3: 78L05 Regulator Schematic

In the schematic for a fixed 78L05 IC regulator, there are multiple parts that serve different roles. Primarily, Q16 (in red), is what controls the current across input-output, and thus controlling the output voltage. The left section (green) serves to keep the circuit away from being stuck in "off" state by providing an initial current to the bandgap circuit with transistor. Then the following bandgap reference section (yellow) maintains stable voltage over a range of temperature conditions by taking the scaled output voltage as input to Q1 and Q6, and checks to see if the output is too high or low by sending the error signal

as input to Q7. Then, this error signal is amplified in the section to the right (orange), and the amplified signal controls the output transistor through Q15, closing the negative feedback loop that controls the output voltage. Throughout the flow, the section in (purple) serves to regulate the temperature from overheating (Q13), excessive input voltage (Q19) and excessive output current (Q14), by lowering the output current and thus protecting from excessive power dissipation damage. The blue section is simply for voltage divider, in which the output voltage is scaled down for bandgap reference input.

Components

- (1) 1 78L05 Fixed Regulator
- (2) 120Ω, Resistors
- (3) 0.01μF, 4.7μF ceramic capacitor
- (4) 1 Power Supply (for fixed 15V and variable supply)
- (5) 1 Oscilloscope

Power Dissipation

 


Figure 4: Power Dissipation

In reference to Figure 3 - Q16 specifically (Figure 4, power dissipation is determined by

$$P_{dissipation} = I_{out}(V_{in} - V_{out}). \quad (1)$$

Ideally, we would like observe the circuit heat sinking when the power dissipation is at maximum, so we determine the maximum allowable input voltage for the power dissipation to be at maximum, by first calculating the maximum value as follows.

$$Power_{maxdissipation} = \frac{T_{junction} - T_{ambient}}{\Theta_{junction-ambient}} \quad (2)$$

where $\Theta_{junction-ambient} = [^{\circ}\text{C}/\text{W}]$ and $T_J, T_A = [^{\circ}\text{C}]$
(for TO-92, plastic package, from datasheet)

We set the ambient(room) temperature to be in $[20, 25]^{\circ}\text{C}$, and take average


to be 23 °C, and then equate the dissipation to be the maximum and determine the maximum input.

$$Power_{maxdissipation} = \frac{150 - 23}{230.9} = 0.55W = \left(\frac{5V}{60\Omega}\right)(V_{in} - 5) \quad (3)$$


Thus $V_{in} \approx 8.3$ Volts. The output voltages at maximum power dissipation (with the determined input voltage of 8.3V) are shown below.

Assumptions

 
- The device begins to limit when its junction temperature reaches ≈ 150 °C



(a) 78L05 Circuit on Breadboard

 

(b) Min V_{out} at max power dissipation

 

(c) Max V_{out} at max power dissipation

Figure 5: At Maximum Power dissipation

The dropout voltage is found to be in range [3.34, 4.915] [Volts] at $V_{in} = 8.3$ Volts that evokes the chip's thermal self-protection. The point at which thermal self-protection action is taken was observed when the output reaches the minimum and no longer is reduced. The chip (as aforementioned in the schematic diagram for the chip) then uses a series of transistors to maintain stable temperature and limit heat dissipation.

$$V_{dropout-1} = V_{in} - V_{out} = 8.3 - 4.96 = 3.34V$$

$$V_{dropout-2} = V_{in} - V_{out} = 8.3 - 3.385 = 4.915V$$

Results

The maximum input voltage value at which the chip activates its thermal self-protection logic was determined and experimentally found to be at around 8.3 Volts, and the range of dropout voltage for the chip was computed to be in [3.34, 4.915] Volt range. An interesting observation was its variations in the output voltage as the chip was cooled down by a fan, changing the maximum input voltage need for thermal self-protection to increase for the maximum power dissipation.

Simulation Results

An LTSpice simulation was done using a subcircuit design of the 78L05 (Appendix A).

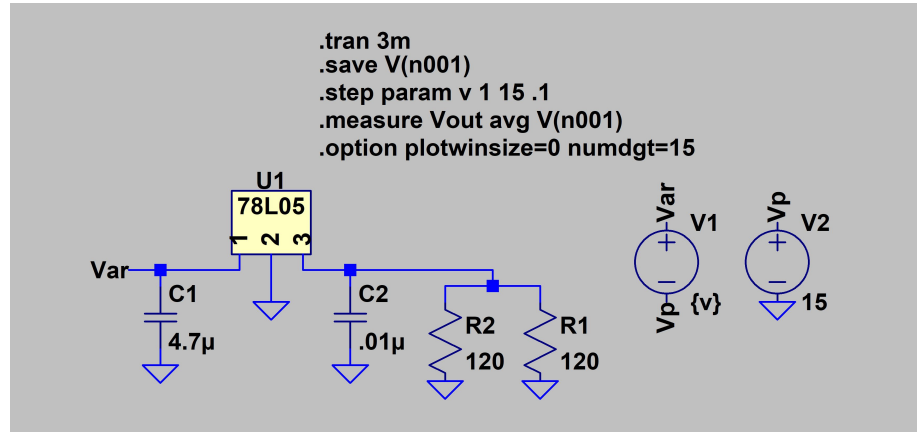


Figure 6: Schematic of LTSpice Simulation

 


Figure 7: Sweep of Voltages from 1V to 15V of the Variable Voltage Source

The range of the output voltage from simulation was 5.04V to 5.05V. This shows that the voltage regulator is able to limit to around 5V when the input is changing.

Summary and Discussion

Upon completion of the experiment it is possible to see the use cases of the three terminal fixed regulator due to how it can be used to regulate the voltage input while maintaining heat dissipation. After calculating the theoretical results of the thermal dissipation, the numbers were tested as voltages which yielded the expected output. Any voltage of 8.3 V or lower on the second power supply would keep the system in equilibrium while any voltage higher would cause the device to thermally throttle, lowering the output voltage and giving off heat. This problem can be fixed in a few different ways such as a heat sink, fanning the regulator, blowing on it and using a wet tissue paper, all of which had caused the self-protection to be unnecessary for the circuit.

2 Lab 12.3 - Adjustable Three-Terminal Regulator: 317

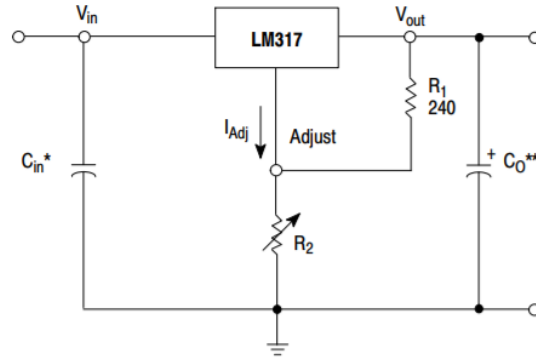


Figure 8: 317 Ad

* C_{in} is required if regulator is located an appreciable distance from power supply filter.

* C_O is not needed for stability, however, it does improve transient response.

Adjustable Three-Terminal Regulator: 317

The LM317 IC regulator chip is an adjustable 3-terminal positive voltage regulator, that can supply in excess of 1.5A over an output voltage range of [1.2, 37] Volts. This chip is also easier to use, as it is similar to a fixed regulator 78L05 with regards to its current and temperature sensing to protect itself from excessive loads (internal current limiting, thermal shutdown and safe area compensation), and also allows to select an output voltage with the addition of two resistors. Furthermore, a variable resistor could allow for a variable output supply. The applications include programmable output regulator and a precision current regulator by connecting a fixed resistor between the adjustment and output.

Components

- (1) 1 LM317-IC-Regulator Chip
- (2) 2 4.7 μ F ceramic capacitors
- (3) 1 240 Ω , 820 Ω Resistors
- (4) 1 Power Supply (for +15 V input)
- (5) 1 Oscilloscope

The output voltage is determined by the following equation.

* Since I_{adj} is controlled to less than 100 A, the error associated with this term is negligible in most applications.

$$v_{out} = 1.25V(1 + \frac{R_2}{R_1}) + I_{adj}R_2 \quad (4)$$

Values	Resistance R [Ω]	Output Range [Volts]
1	820	5.81
2	1k POT	[1.241, 6.91]
3	0	1.241

Results

As expected, for a certain resistance value, the output voltage varied accordingly. Since the chip is designed to return an output voltage from range of [1.2, 37] Volts, the lowest with $R = 0$ of 1.241 Volts makes sense, and as the resistance is increased, the ratio of R_2 and R_1 is also increased, thereby increasing the output voltage overall.

Simulation Results

An LTSpice simulation was done using a subcircuit design of the LM317 (Appendix B).

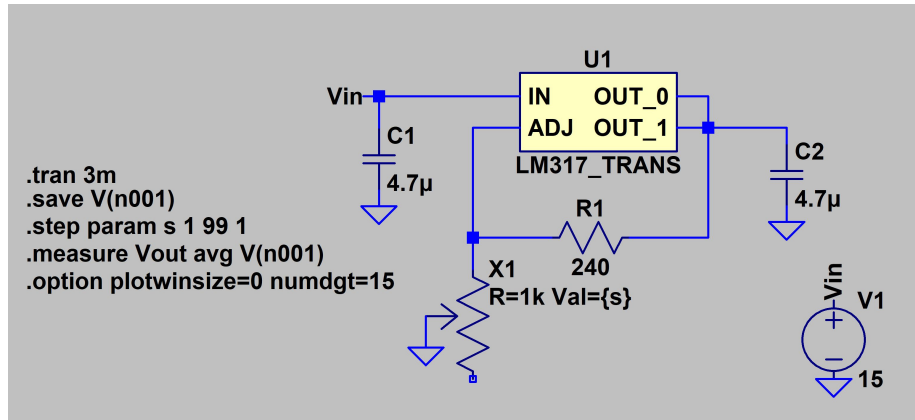


Figure 9: Schematic of LTSpice Simulation

 


Figure 10: V_{out} , $R = 750 \, \Omega$



Figure 11: V_{out} with R sweep

Summary and Discussion

Based on the experimental results, the way that the circuit performs is as expected since the combination of resistors leads to different values for the output voltage. While the regulator has similar properties to the 78L05 in that both include current and temperature sensors to protect from overloads, that component of the 317 was not tested as it was already deemed to be accurate in the previous part of this experiment concerning the 78L05.

3 Lab 12.5 - "Crowbar" Over-Voltage Protection

 


Figure 12: "Crowbar" Over-Voltage Protection

"Crowbar" Over-Voltage Protection

"Crowbar" circuit is simply a circuit that shuts down the supply when the voltage climb is too high. For example, the Figure 12 shows a circuit consisted of a Zener diode and a resistor in series, and a thyristor (Silicon Controlled Rectifier, SCR) in parallel. When the voltage climb reaches above ≈ 5 Volts, the Zener diode begins to conduct, and when the voltage across the 100Ω resistor reaches ≈ 0.6 Volts (threshold), the thyristor activates, clamping the supply to ground. In a more practical configuration, a capacitor would be added at the gate of the SCR, to protect from triggering on brief transients.

Zener Diode

A Zener diode is a one-way current-conducting device that has a region in its reverse bias characteristics of almost a constant negative voltage regardless of the value of the current flowing through the diode, and maintains constant constant current even with large changes as far as the current remains between the breakdown current (min) and the maximum current rating (max). Zener Diodes can be used to produce a stable voltage output with low ripple under varying load current conditions. By passing a small current through the diode from a voltage source, via a suitable current limiting resistor, the zener diode will conduct sufficient current to maintain a voltage drop of V_{out} .

Thyristor

A thyristor is a semiconductor device with four layers of P-type and N-type bases. It serves as a bistable switch, conducting when the gate receives a current trigger and continuing to conduct until the voltage across the device is reverse-biased or removed. A 3-terminal thyristor is aimed to control the larger current from the anode to cathode by controlling the gate current (smaller). In contrast, while a 2lead thyristor is designed to turn on when the voltage across the two terminals becomes sufficiently large (breakdown voltage).

A thyristor have 3 states of operation:

- (1) Reverse blocking mode: Voltage is applied in the direction that would be

blocked by a diode

(2) Forward blocking mode: Voltage is applied in the direction that would cause a diode to conduct, but the thyristor has not been triggered into conduction

(3) Forward conducting mode: The thyristor has been triggered into conduction and will remain conducting until the forward current drops below a threshold value known as the "holding current"

 


Figure 13: Thyristor

In summary, a thyristor operates as follows:

- A small gate current controls a larger anode current
- Conducts current only in forward-bias and triggers current applied at the gate
- Behaves like a rectifying diode once it is triggered ON
- Anode current must be greater than "holding current" to maintain conduction
- Blocks current flow when reverse biased, no matter if gate current is applied
- Once triggered ON, it will be latched ON conducting even when a gate current is no longer applied providing anode current is above "latching current".

 


Figure 14: Comparison between Zener diode and SCR I/V Characteristics

Components

- (1) 1 1N759A Zener diode
- (2) 1 11C106D Thyristor (Silicon Controlled Rectifier)
- (3) 0.1 μ F Capacitor
- (4) 1 Power Supply (for +15 V, -15 V, GND)
- (5) 1 Oscilloscope

The measurements taken at the supply and gate describe the behavior of the "crowbar" regulator circuit. As the supply voltage is increased up to 12.5 V (1st data point), the gate voltage remains below the threshold of 0.6 V, and thus the supply is maintained as what was adjusted at the input. However, a slight more increase of the supply causes clamping of the supply to almost ground, upon the gate voltage going over the threshold voltage of the Zener diode. Therefore upon triggering with input greater than 12.5 V causes the 2nd data point to be pulled down to the minimum supply voltage (minimum of the observed varying data) due to the protection measure of the circuit by the SCR.

	Supply Voltage	Gate Voltage
1	12.5 V (max)	0.5 V
2	1.0 V (min)	0.8 V

Simulation Results

An LTSpice simulation was done using a subcircuit design of a thyristor (Appendix C).

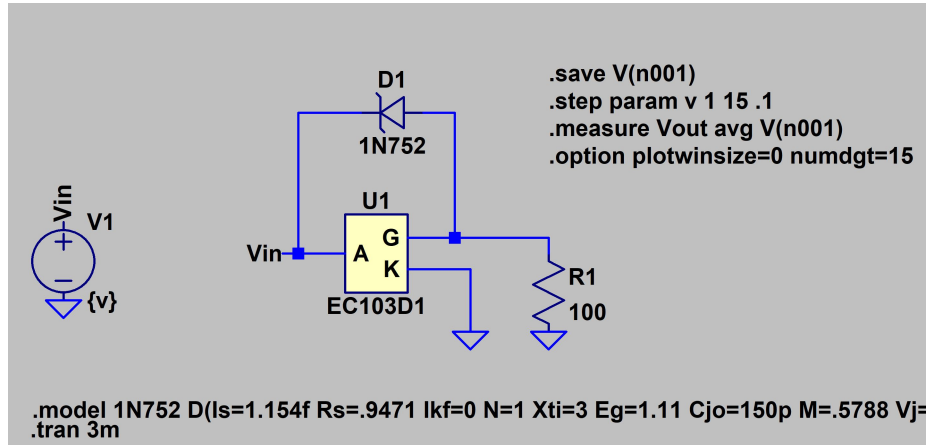


Figure 15: Schematic of LTSpice Simulation

 


Figure 16: V_{gate} increases as V_{supply} increases

As seen in the experiment, the gate voltage of SCR increased once the input voltage reached a certain point.

Summary and Discussion

In this experiment, the thyristor was tested to show the "crowbar" over-voltage protection circuit and how there exists a boundary in the amount of input voltage the device can handle before it begins conducting, causing the device to be in its "ON State" as shown in Figure 9b with the holding current. Experimentally this voltage was discovered after increasing the voltage to 12.5 V which is the upper boundary of the input voltage which had decreased to 1.0 V when attempting to increase any further, indicating the lower bound of the input voltage.

Overall Conclusions

From experimenting with fixed- and adjustable- voltage regulators using 78L05 and LM317, as well as a "crowbar" circuit with a Zener diode and a thyristor (SCR), means of controlling the voltage given a variable supply voltage and parameters such as power dissipation have been explored. Determination of the point of failure, current at its "latching" and "holding" states for SCR, and understanding of sub-circuits that serve to minimize damage and protect from excessive heat sinking allowed to apply these acquired design considerations to a larger application.

Appendix A 78L05 Design

```

1 *****
2 *dummy subckt used only for symbol initialization
3 .subckt Vreg 1 2 3
4 .ends
5 *****

6 .subckt 7805 In Aj Out
7 F1 In 0 Vc 1
8 Rcon In 0 1e6
9 B1 4 Aj V= Table (V(In,Aj), 0,0, 1,0, 7,5, 35,5, 36,0)
10 Vc 4 Out 0
11 F2 In Aj Vc 4m
12 .ends
13 *78L05 MCE 7-12-95
14 *78L05 circuit taken from Signetics 1977 Analog Data Book page 160
15 *5V 100mA Voltage Regulator pkg:TO-92 1,2,3
16 .SUBCKT 78L05 1 2 3
17 Q1 5 5 1 QPNP
18 Q2 10 5 1 QPNP
19 Q3 1 11 12 QNPN
20 Q4 1 10 11 QNPN
21 Q5 10 13 14 QNPN
22 Q6 1 4 20 QNPN
23 Q7 10 19 21 QNPN
24 Q8 9 9 2 QNPN
25 Q9 18 9 22 QNPN OFF
26 Q10 8 18 2 QNPN
27 Q11 5 7 17 QNPN
28 Q12 5 16 17 QNPN
29 Q13 10 15 17 QNPN
30 C1 15 10 20E-12
31 D1 2 4 DZ5V
32 Q14 2 8 7 QPNP
33 R17 2 17 4E3
34 R16 4 1 20E3
35 R15 16 20 4E3
36 R14 19 16 700
37 R13 2 19 300
38 R12 2 21 100
39 R11 9 7 1E3
40 R10 18 7 10E3
41 R9 7 3 2.2E3
42 R8 2 22 1E3
43 R7 8 7 2E3
44 R6 2 15 1.4E3
45 R5 15 3 4.5E3
46 R4 3 14 100
47 R3 3 12 2
48 R2 13 11 500
49 R1 13 12 200
50
51 .MODEL QPNP PNP(IS=1.05E-15 BF=220 VAF=240 IKF=0.1 ISE=1.003E-9
52 + NE=4 ISC=1.003E-9 NC=4 RB=3 RE=0.5 RC=0.2 CJE=5.7E-12 VJE=0.75 TF
   =3.35E-10

```

```

53 + CJC=4.32E-12 VJC=0.75 TR=1.7E-7 VJS=0.75 KF=4E-15 )
54
55 .MODEL QNPN NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11
56 + NE=2 BR=4 VAR=24 IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11
57 + TF=3.97E-10 CJC=1.52E-11 TR=8.5E-8 XTB=1.5 )
58
59 .MODEL DZ5V D(IS=1E-11 RS=7.708 N=1.27 TT=5E-8 CJO=4.068E-10 VJ
    =0.75
60 + M=0.33 BV=4.946 IBV=0.01 )
61 .ENDS 78L05
62 * LM7805 model.
63 * No need to use .inc - I've set the .asy symbol to remove the need
    for .inc.
64 * (I used the symbol of LT1084, just replaced the LT1084 by LMxxxx
    and LTC.LIB by regulators.lib)
65
66 .SUBCKT LM7805 1 2 3
67 * In GND Out
68 QT6 23 10 2 Q_NPN 0.1
69 QT7 5 4 10 Q_NPN 0.1
70 QT5 7 6 5 Q_NPN 0.1
71 QT1 1 9 8 Q_NPN 0.1
72 QT3 11 8 7 Q_NPN 0.1
73 QT2 11 13 12 Q_NPN 0.1
74 QT17 1 15 14 Q_NPN 10
75 C2 10 23 4P
76 R16 12 5 500
77 R12 16 2 12.1K
78 QT18 17 23 16 Q_NPN 0.1
79 D1 18 19 D.D
80 R11 20 21 850
81 R5 22 3 100
82 QT14 24 18 2 Q_NPN 0.1
83 R21 6 2 2.67K
84 R20 3 6 640
85 DZ2 25 26 D_5V1
86 R19 1 26 16K
87 R18 14 3 250M
88 R17 25 14 380
89 R15 25 15 1.62K
90 QT16 1 20 15 Q_NPN 1
91 QT15 2 24 21 Q_PNP 0.1
92 *OFF
93 R14 21 24 4K
94 C1 27 24 20P
95 R13 19 2 4K
96 QT13 24 27 18 Q_NPN 0.1
97 QT12 20 25 22 Q_NPN 1
98 *OFF
99 QT11 20 28 2 Q_NPN 0.1
100 *OFF
101 QT10 20 11 1 Q_PNP 0.1
102 R10 17 27 16.5K
103 R9 5 4 1.9K
104 R8 4 23 26
105 R7 10 2 1.2K
106 R6 29 2 1K

```



```

107 QT9          11  11  1  Q_PNP 0.1
108 QT8          27  16  29 Q_NPN 0.1
109 QT4          15  6   17 Q_NPN 0.1
110 DZ1          2   9      D_5V6
111 R4            1   9      80K
112 R3           28  2      830
113 R2           13  28     4.97K
114 R1            8  13      7K
115 *
116 .MODEL D_5V1 D( IS=10F N=1.16 BV=5.1 IBV=0.5M CJO = 1P TT = 10p )
117 .MODEL D_5V6 D( IS=10F N=1.16 BV=5.6 IBV=5U CJO = 1P TT = 10p )
118 .MODEL Q_NPN NPN( IS=10F NF=1.16 NR=1.16 BF=80 CJC=1P CJE=2P
119 +      TF=10P TR=1N )
120 .MODEL Q_PNP PNP( IS=10F NF=1.16 NR=1.16 BF=80 CJC=1P CJE=2P
121 +      TF=10P TR=1N )
122 .MODEL D_D D( IS=1F N=1.16 CJO = 1P TT = 10p )
123
124 .ENDS LM7805
125 *
126 *=====

```

Appendix B LM317 Design

```

1  * PSpice Model Editor – Version 16.2.0
2  *$
3  * LM317
4  *****

5  * (C) Copyright 2014 Texas Instruments Incorporated. All rights
   reserved.
6  *****

7  ** This model is designed as an aid for customers of Texas
   Instruments.
8  ** TI and its licensors and suppliers make no warranties, either
   expressed
9  ** or implied, with respect to this model, including the warranties
   of
10 ** merchantability or fitness for a particular purpose. The model
   is
11 ** provided solely on an "as is" basis. The entire risk as to its
   quality
12 ** and performance is with the customer.
13 *****

14 *
15 ** Released by: WEBENCH Design Center, Texas Instruments Inc.
16 * Part: LM317
17 * Date: 11DEC2014
18 * Model Type: TRANSIENT
19 * Simulator: PSPICE
20 * Simulator Version: 16.2.0.p001
21 * EVM Order Number:
22 * EVM Users Guide:
23 * Datasheet:SLVS044VSEPTEMBER 1997REVISED FEBRUARY 2013
24 *
25 * Model Version: Final 1.00

```

```

26 *
27 *****

28 *
29 * Updates:
30 *
31 * Final 1.00
32 * Release to Web
33 *
34 *****

35 .SUBCKT LM317_TRANS IN ADJ OUT_0 OUT_1
36 R_R1      VXX IN  {RINP}
37 R_R6      N242982 VYY 10 TC=0,0
38 R_R5      VZZ VYY {ROUT}
39 E_ABM1     N242982 0 VALUE { MIN(V(VXX), (V(Vzz)+(ILIM*ROUT)))
      }
40 R_R2      N222524 VXX {PSRR*RINP}
41 R_U1_R2    0 U1_N26728 1G
42 E_U1_ABM5  U1_N31197 0 VALUE { MIN(V(U1_N26728),
43 + MAX(V(IN) - {DROP}, 0)) }
44 C_U1_C2    0 U1_N26728 1n
45 R_U1_R1    0 U1_N08257 1G
46 R_U1_R4    U1_N28933 U1_N26728 10 TC=0,0
47 R_U1_R5    U1_N31197 N222524 10 TC=0,0
48 C_U1_C3    0 N222524 1n
49 X_U1_U2    IN U1_N12783 U1_N12664 U1_UVLO_OK COMPHYS_BASIC_GEN
      PARAMS:
50 + VDD=1 VSS=0 VTHRESH=0.5
51 C_U1_C1    0 U1_N08257 {1e-6*SQRT(TTRN)}
52 V_U1_V4    U1_N12783 0 {UVLO}
53 V_U1_V3    U1_N12664 0 {UHYS}
54 E_U1_ABM6  U1_EN_OUT 0 VALUE { IF(V(U1_UVLO_OK)> 0.6, {VREF
      }, 0) }
55 R_U1_R3    U1_EN_OUT U1_N08257 {3.333e5*SQRT(TTRN)} TC=0,0
56 E_U1_ABM4  U1_N28933 0 VALUE { V(U1_N08257)*
57 + (ABS(V(OUT_0))/(ABS(V(OUT_0)-v(ADJ)))) }
58 X_U2      0 OUT_0 d_d PARAMS:
59 X_F1      VZZ OUT_0 IN VYY LM317_TRANS_F1
60 C_C1      VXX IN {1/(6.28*RINP*POLE)}
61 C_C2      VXX N222524 {1/(6.28*PSRR*RINP*ZERO)}
62 C_C3      0 VYY 1n
63 .PARAM psrr=7.9432e-4 uvlo=0 ilim=2.2 pole=15k rinp=1e7 zero=100e6
      rout=0.4m
64 + ttrn=1e-4 vref=1.25 uhys=0 drop=.5
65 .ENDS LM317_TRANS
66 *$
67 .SUBCKT LM317_TRANS_F1 1 2 3 4
68 F_F1      3 4 VF_F1 1
69 VF_F1     1 2 0V
70 .ENDS LM317_TRANS_F1
71 *$
72 .SUBCKT COMP_BASIC_GEN INP INM Y PARAMS: VDD=1 VSS=0 VTHRESH=0.5
73 E_ABM Yint 0 VALUE {IF (V(INP) >
74 + V(INM), {VDD},{VSS})}
75 R1 Yint Y 1
76 C1 Y 0 1n

```

```

77 .ENDS COMP_BASIC_GEN
78 *$
79 .SUBCKT COMPHYS_BASIC_GEN INP INM HYS OUT PARAMS: VDD=1 VSS=0
      VTHRESH=0.5
80 EIN INP1 INM1 INP INM 1
81 EHYS INP1 INP2 VALUE { IF( V(1) > {VTHRESH},-V(HYS),0) }
82 EOUT OUT 0 VALUE { IF( V(INP2)>V(INM1), {VDD} ,{VSS}) }
83 R1 OUT 1 1
84 C1 1 0 5n
85 RINP1 INP1 0 1K
86 .ENDS COMPHYS_BASIC_GEN
87 *$
88 .SUBCKT COMPHYS2_BASIC_GEN INP INM HYS OUT PARAMS: VDD=1 VSS=0
      VTHRESH=0.5
89 + T=10
90 EIN INP1 INM1 INP INM 1
91 EHYS INM2 INM1 VALUE { IF( V(1) > {VTHRESH},-V(HYS)/2,V(HYS)/2) }
92 EOUT OUT 0 VALUE { IF( V(INP1)>V(INM2), {VDD} ,{VSS}) }
93 R1 OUT 1 1
94 C1 1 0 {T*1e-9}
95 RINP1 INP1 0 10K
96 RINM2 INM2 0 10K
97 .ENDS COMPHYS2_BASIC_GEN
98 *$
99 .SUBCKT D_D 1 2
100 D1 1 2 DD
101 .MODEL DD D (IS=1E-015 N=0.01 TT=1e-011)
102 .ENDS D_D
103 *$

```

Appendix C Thyristor (SCR) Design

```

1 *****
2 *****
3 **
4 ** Littelfuse , LP
5 ** SCR SPICE Models
6 ** EC103xx-SxSx
7 **
8 ** T. Chenoski
9 ** Irving Technical Center
10 **
11 ** A 06/13/08
12 **
13 *****
14 *****
15 .SUBCKT EC103D1      1  2      3
16 *      TERMINALS:  A  G      K
17 Qpnp   6      4  1      Pfor   OFF
18 Qnpn   4      6  5      Nfor   OFF
19 Rfor   6      4  5G
20 Rrev   1      4  5G
21 Rshort 6      5  1MEG
22 Rlat   2      6  9.09
23 Ron    3      5  513.4m
24 Dfor   6      4  Zbrk

```

```

25 Drev      1          4 Zbrk
26 Dgate     6          5 Zgate
27 .MODEL    Zbrk      D (IS=3.2E-16 IBV=100U BV=400)
28 .MODEL    Zgate     D (IS=1E-16   IBV=100U BV=10   VJ=0.3)
29 .MODEL    Pfor      PNP( IS=5E-15   BF=6.10 CJE=5p   CJC=2p
      TF=0.3U)
30 .MODEL    Nfor      NPN( IS=1E-12   ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
31 .ENDS
32
33 .SUBCKT   EC103M1    1  2          3
34 *        TERMINALS: A  G          K
35 Qpnp     6          4  1          Pfor      OFF
36 Qnpn     4          6  5          Nfor      OFF
37 Rfor     6          4  5G
38 Rrev     1          4  5G
39 Rshort   6          5  1MEG
40 Rlat     2          6  9.09
41 Ron      3          5  513.4m
42 Dfor     6          4  Zbrk
43 Drev     1          4  Zbrk
44 Dgate    6          5  Zgate
45 .MODEL    Zbrk      D (IS=3.2E-16 IBV=100U BV=600)
46 .MODEL    Zgate     D (IS=1E-16   IBV=100U BV=10   VJ=0.3)
47 .MODEL    Pfor      PNP( IS=5E-15   BF=6.10 CJE=5p   CJC=2p
      TF=0.3U)
48 .MODEL    Nfor      NPN( IS=1E-12   ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
49 .ENDS
50
51 .SUBCKT   EC103D2    1  2          3
52 *        TERMINALS: A  G          K
53 Qpnp     6          4  1          Pfor      OFF
54 Qnpn     4          6  5          Nfor      OFF
55 Rfor     6          4  5G
56 Rrev     1          4  5G
57 Rshort   6          5  1MEG
58 Rlat     2          6  9.09
59 Ron      3          5  513.4m
60 Dfor     6          4  Zbrk
61 Drev     1          4  Zbrk
62 Dgate    6          5  Zgate
63 .MODEL    Zbrk      D (IS=3.2E-16 IBV=100U BV=400)
64 .MODEL    Zgate     D (IS=1E-16   IBV=100U BV=10   VJ=0.3)
65 .MODEL    Pfor      PNP( IS=5E-15   BF=2.20 CJE=5p   CJC=2p
      TF=0.3U)
66 .MODEL    Nfor      NPN( IS=1E-12   ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
67 .ENDS
68
69 .SUBCKT   EC103M2    1  2          3
70 *        TERMINALS: A  G          K
71 Qpnp     6          4  1          Pfor      OFF
72 Qnpn     4          6  5          Nfor      OFF
73 Rfor     6          4  5G
74 Rrev     1          4  5G
75 Rshort   6          5  1MEG

```

```

76 Rlat      2          6  9.09
77 Ron       3          5  513.4m
78 Dfor      6          4  Zbrk
79 Drev      1          4  Zbrk
80 Dgate     6          5  Zgate
81 .MODEL    Zbrk      D  ( IS=3.2E-16  IBV=100U  BV=600)
82 .MODEL    Zgate     D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
83 .MODEL    Pfor      PNP( IS=5E-15    BF=2.20  CJE=5p   CJC=2p
      TF=0.3U)
84 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)
85 .ENDS
86
87 .SUBCKT   EC103D      1  2          3
88 *         TERMINALS: A  G          K
89 Qpnp      6          4  1          Pfor      OFF
90 Qnpn      4          6  5          Nfor      OFF
91 Rfor      6          4  5G
92 Rrev      1          4  5G
93 Rshort    6          5  1MEG
94 Rlat      2          6  9.09
95 Ron       3          5  513.4m
96 Dfor      6          4  Zbrk
97 Drev      1          4  Zbrk
98 Dgate     6          5  Zgate
99 .MODEL    Zbrk      D  ( IS=3.2E-16  IBV=100U  BV=400)
100 .MODEL    Zgate     D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
101 .MODEL    Pfor      PNP( IS=5E-15    BF=1.10  CJE=5p   CJC=2p
      TF=0.3U)
102 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)
103 .ENDS
104
105 .SUBCKT   EC103M      1  2          3
106 *         TERMINALS: A  G          K
107 Qpnp      6          4  1          Pfor      OFF
108 Qnpn      4          6  5          Nfor      OFF
109 Rfor      6          4  5G
110 Rrev      1          4  5G
111 Rshort    6          5  1MEG
112 Rlat      2          6  9.09
113 Ron       3          5  513.4m
114 Dfor      6          4  Zbrk
115 Drev      1          4  Zbrk
116 Dgate     6          5  Zgate
117 .MODEL    Zbrk      D  ( IS=3.2E-16  IBV=100U  BV=600)
118 .MODEL    Zgate     D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
119 .MODEL    Pfor      PNP( IS=5E-15    BF=1.10  CJE=5p   CJC=2p
      TF=0.3U)
120 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)
121 .ENDS
122
123 .SUBCKT   EC103D3     1  2          3
124 *         TERMINALS: A  G          K
125 Qpnp      6          4  1          Pfor      OFF
126 Qnpn      4          6  5          Nfor      OFF

```

```

127 Rfor      6          4  5G
128 Rrev      1          4  5G
129 Rshort    6          5  1MEG
130 Rlat      2          6  9.09
131 Ron       3          5  513.4m
132 Dfor      6          4  Zbrk
133 Drev      1          4  Zbrk
134 Dgate     6          5  Zgate
135 .MODEL    Zbrk      D  (IS=3.2E-16  IBV=100U  BV=400)
136 .MODEL    Zgate     D  (IS=1E-16    IBV=100U  BV=10    VJ=0.3)
137 .MODEL    Pfor      PNP( IS=5E-15    BF=0.95  CJE=5p    CJC=2p
      TF=0.3U)
138 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
139 .ENDS
140
141 .SUBCKT   EC103M3    1  2          3
142 *        TERMINALS: A  G          K
143 Qpnp      6          4  1          Pfor      OFF
144 Qnpn      4          6  5          Nfor      OFF
145 Rfor      6          4  5G
146 Rrev      1          4  5G
147 Rshort    6          5  1MEG
148 Rlat      2          6  9.09
149 Ron       3          5  513.4m
150 Dfor      6          4  Zbrk
151 Drev      1          4  Zbrk
152 Dgate     6          5  Zgate
153 .MODEL    Zbrk      D  (IS=3.2E-16  IBV=100U  BV=600)
154 .MODEL    Zgate     D  (IS=1E-16    IBV=100U  BV=10    VJ=0.3)
155 .MODEL    Pfor      PNP( IS=5E-15    BF=0.95  CJE=5p    CJC=2p
      TF=0.3U)
156 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
157 .ENDS
158
159 .SUBCKT   S4S1       1  2          3
160 *        TERMINALS: A  G          K
161 Qpnp      6          4  1          Pfor      OFF
162 Qnpn      4          6  5          Nfor      OFF
163 Rfor      6          4  5G
164 Rrev      1          4  5G
165 Rshort    6          5  1MEG
166 Rlat      2          6  9.09
167 Ron       3          5  513.4m
168 Dfor      6          4  Zbrk
169 Drev      1          4  Zbrk
170 Dgate     6          5  Zgate
171 .MODEL    Zbrk      D  (IS=3.2E-16  IBV=100U  BV=400)
172 .MODEL    Zgate     D  (IS=1E-16    IBV=100U  BV=10    VJ=0.3)
173 .MODEL    Pfor      PNP( IS=5E-15    BF=6.10  CJE=5p    CJC=2p
      TF=0.3U)
174 .MODEL    Nfor      NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
175 .ENDS
176
177 .SUBCKT   S6S1       1  2          3

```

```

178 *      TERMINALS: A  G      K
179 Qpnp    6      4  1      Pfor    OFF
180 Qnpn    4      6  5      Nfor    OFF
181 Rfor    6      4  5G
182 Rrev    1      4  5G
183 Rshort  6      5  1MEG
184 Rlat    2      6  9.09
185 Ron     3      5  513.4m
186 Dfor    6      4  Zbrk
187 Drev    1      4  Zbrk
188 Dgate   6      5  Zgate
189 .MODEL  Zbrk    D  ( IS=3.2E-16  IBV=100U  BV=600)
190 .MODEL  Zgate   D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
191 .MODEL  Pfor    PNP( IS=5E-15    BF=6.10   CJE=5p   CJC=2p
      TF=0.3U)
192 .MODEL  Nfor    NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)
193 .ENDS
194
195 .SUBCKT S4S2      1  2      3
196 *      TERMINALS: A  G      K
197 Qpnp    6      4  1      Pfor    OFF
198 Qnpn    4      6  5      Nfor    OFF
199 Rfor    6      4  5G
200 Rrev    1      4  5G
201 Rshort  6      5  1MEG
202 Rlat    2      6  9.09
203 Ron     3      5  513.4m
204 Dfor    6      4  Zbrk
205 Drev    1      4  Zbrk
206 Dgate   6      5  Zgate
207 .MODEL  Zbrk    D  ( IS=3.2E-16  IBV=100U  BV=400)
208 .MODEL  Zgate   D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
209 .MODEL  Pfor    PNP( IS=5E-15    BF=2.20   CJE=5p   CJC=2p
      TF=0.3U)
210 .MODEL  Nfor    NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)
211 .ENDS
212
213 .SUBCKT S6S2      1  2      3
214 *      TERMINALS: A  G      K
215 Qpnp    6      4  1      Pfor    OFF
216 Qnpn    4      6  5      Nfor    OFF
217 Rfor    6      4  5G
218 Rrev    1      4  5G
219 Rshort  6      5  1MEG
220 Rlat    2      6  9.09
221 Ron     3      5  513.4m
222 Dfor    6      4  Zbrk
223 Drev    1      4  Zbrk
224 Dgate   6      5  Zgate
225 .MODEL  Zbrk    D  ( IS=3.2E-16  IBV=100U  BV=600)
226 .MODEL  Zgate   D  ( IS=1E-16    IBV=100U  BV=10   VJ=0.3)
227 .MODEL  Pfor    PNP( IS=5E-15    BF=2.20   CJE=5p   CJC=2p
      TF=0.3U)
228 .MODEL  Nfor    NPN( IS=1E-12    ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p      TF=0.3U)

```

```

229 .ENDS
230
231 .SUBCKT S4S      1  2      3
232 *      TERMINALS: A  G      K
233 Qpnp    6      4  1      Pfor    OFF
234 Qnpn    4      6  5      Nfor    OFF
235 Rfor    6      4  5G
236 Rrev    1      4  5G
237 Rshort  6      5  1MEG
238 Rlat    2      6  9.09
239 Ron     3      5  513.4m
240 Dfor    6      4  Zbrk
241 Drev    1      4  Zbrk
242 Dgate   6      5  Zgate
243 .MODEL  Zbrk    D  (IS=3.2E-16  IBV=100U  BV=400)
244 .MODEL  Zgate   D  (IS=1E-16   IBV=100U  BV=10   VJ=0.3)
245 .MODEL  Pfor    PNP( IS=5E-15   BF=1.10  CJE=5p   CJC=2p
      TF=0.3U)
246 .MODEL  Nfor    NPN( IS=1E-12   ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
247 .ENDS
248
249 .SUBCKT S6S      1  2      3
250 *      TERMINALS: A  G      K
251 Qpnp    6      4  1      Pfor    OFF
252 Qnpn    4      6  5      Nfor    OFF
253 Rfor    6      4  5G
254 Rrev    1      4  5G
255 Rshort  6      5  1MEG
256 Rlat    2      6  9.09
257 Ron     3      5  513.4m
258 Dfor    6      4  Zbrk
259 Drev    1      4  Zbrk
260 Dgate   6      5  Zgate
261 .MODEL  Zbrk    D  (IS=3.2E-16  IBV=100U  BV=600)
262 .MODEL  Zgate   D  (IS=1E-16   IBV=100U  BV=10   VJ=0.3)
263 .MODEL  Pfor    PNP( IS=5E-15   BF=1.10  CJE=5p   CJC=2p
      TF=0.3U)
264 .MODEL  Nfor    NPN( IS=1E-12   ISE=1E-9  BF=10.0  RC=0.45
      CJE=30p  CJC=2p    TF=0.3U)
265 .ENDS
266
267 .SUBCKT S4S3     1  2      3
268 *      TERMINALS: A  G      K
269 Qpnp    6      4  1      Pfor    OFF
270 Qnpn    4      6  5      Nfor    OFF
271 Rfor    6      4  5G
272 Rrev    1      4  5G
273 Rshort  6      5  1MEG
274 Rlat    2      6  9.09
275 Ron     3      5  513.4m
276 Dfor    6      4  Zbrk
277 Drev    1      4  Zbrk
278 Dgate   6      5  Zgate
279 .MODEL  Zbrk    D  (IS=3.2E-16  IBV=100U  BV=400)
280 .MODEL  Zgate   D  (IS=1E-16   IBV=100U  BV=10   VJ=0.3)
281 .MODEL  Pfor    PNP( IS=5E-15   BF=0.95  CJE=5p   CJC=2p

```



```

                TF=0.3U)
282 .MODEL      Nfor      NPN( IS=1E-12      ISE=1E-9   BF=10.0      RC=0.45
                CJE=30p    CJC=2p          TF=0.3U)
283 .ENDS
284
285 .SUBCKT S6S3      1  2      3
286 *      TERMINALS: A  G      K
287 Qpnp    6      4  1      Pfor      OFF
288 Qnpn    4      6  5      Nfor      OFF
289 Rfor    6      4  5G
290 Rrev    1      4  5G
291 Rshort  6      5  1MEG
292 Rlat    2      6  9.09
293 Ron     3      5  513.4m
294 Dfor    6      4  Zbrk
295 Drev    1      4  Zbrk
296 Dgate   6      5  Zgate
297 .MODEL  Zbrk      D  ( IS=3.2E-16   IBV=100U   BV=600)
298 .MODEL  Zgate     D  ( IS=1E-16     IBV=100U   BV=10      VJ=0.3)
299 .MODEL  Pfor      PNP( IS=5E-15     BF=0.95   CJE=5p     CJC=2p
                TF=0.3U)
300 .MODEL      Nfor      NPN( IS=1E-12      ISE=1E-9   BF=10.0      RC=0.45
                CJE=30p    CJC=2p          TF=0.3U)
301 .ENDS

```